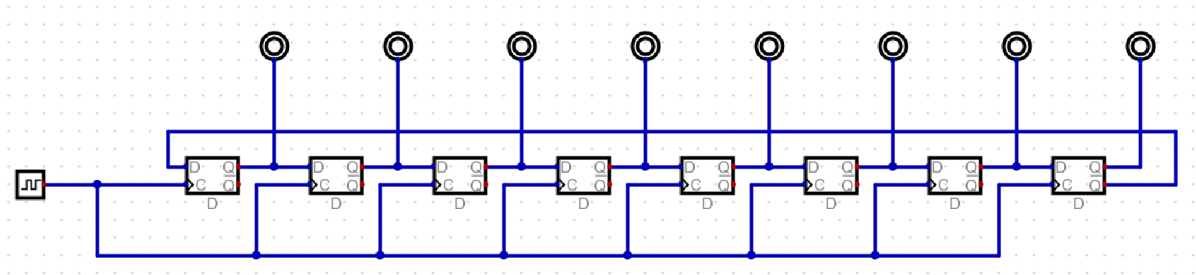


# 8-bit Johnson Counter

Johnson counter, also known as creeping counter, is an example of a synchronous counter. In the Johnson counter, the complemented output of the last flip flop is connected to the input of the first flip flop, and to implement the n-bit Johnson counter; we require n flip-flop. It is one of the essential types of shift register counter. It is formed by the feedback of the output to its own input.

Johnson counter is a ring with an inversion. Another name of the Johnson counter is creeping counter, twisted ring counter, walking counter, mobile counter, and switch tail counter.

**Circuit Diagram**



**Truth Table**

Clock Pulse	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8
1	0	0	0	0	0	0	0	0
2	1	0	0	0	0	0	0	0
3	1	1	0	0	0	0	0	0
4	1	1	1	0	0	0	0	0
5	1	1	1	1	0	0	0	0
6	1	1	1	1	1	0	0	0
7	1	1	1	1	1	1	0	0
8	1	1	1	1	1	1	1	0
9	1	1	1	1	1	1	1	1
10	0	1	1	1	1	1	1	1
11	0	0	1	1	1	1	1	1
12	0	0	0	1	1	1	1	1
13	0	0	0	0	1	1	1	1
14	0	0	0	0	0	1	1	1
15	0	0	0	0	0	0	1	1
16	0	0	0	0	0	0	0	1
17	0	0	0	0	0	0	0	0